



MUNICH, GERMANY  
OCTOBER 14-15, 2025

# A UVM Testbench for Exploring Design Margins of Analog/Mixed-Signal Systems: A PCI-Express Receiver Detection Circuit Example

Jaeha Kim


Seoul National University / Scientific Analog, Inc.

scientific analog



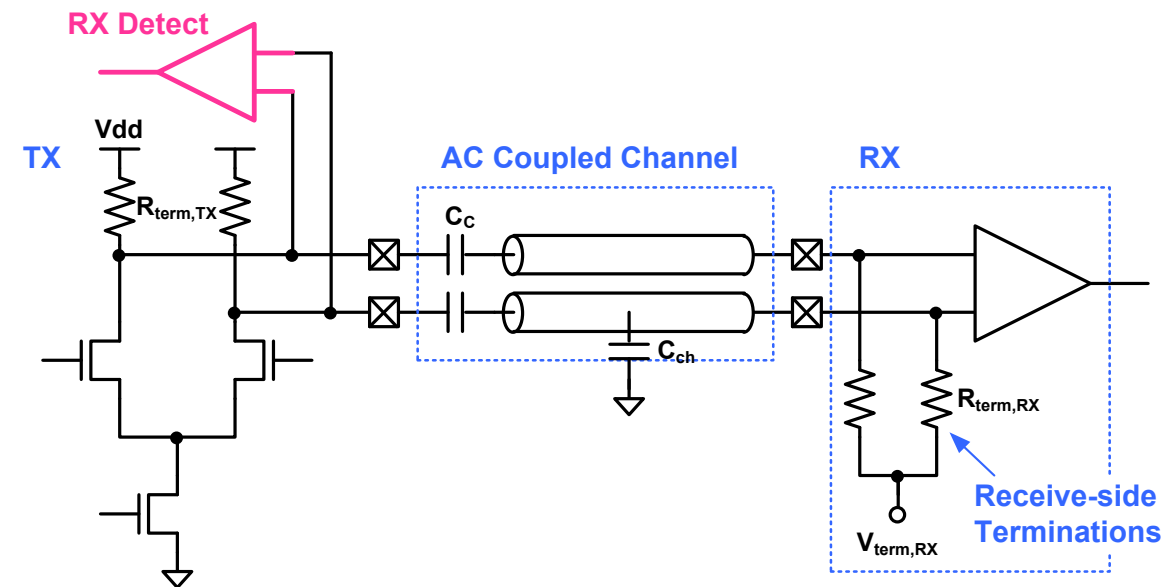
# PCIe Receiver Detection Circuit

- A PCIe transmitter (TX) needs to determine whether a receiver (RX) is connected before initiating data transmission
- The receiver detection circuit must function correctly for a range of condition parameters:
  - AC coupling capacitance ( $C_c$ ) : 76~265nF
  - Equiv. channel capacitance ( $C_{ch}$ ) : 0~3nF
  - TX-side termination ( $R_{term,TX}$ ) : 40~60 $\Omega$
  - RX-side termination ( $R_{term,RX}$ ) : 40~60 $\Omega$


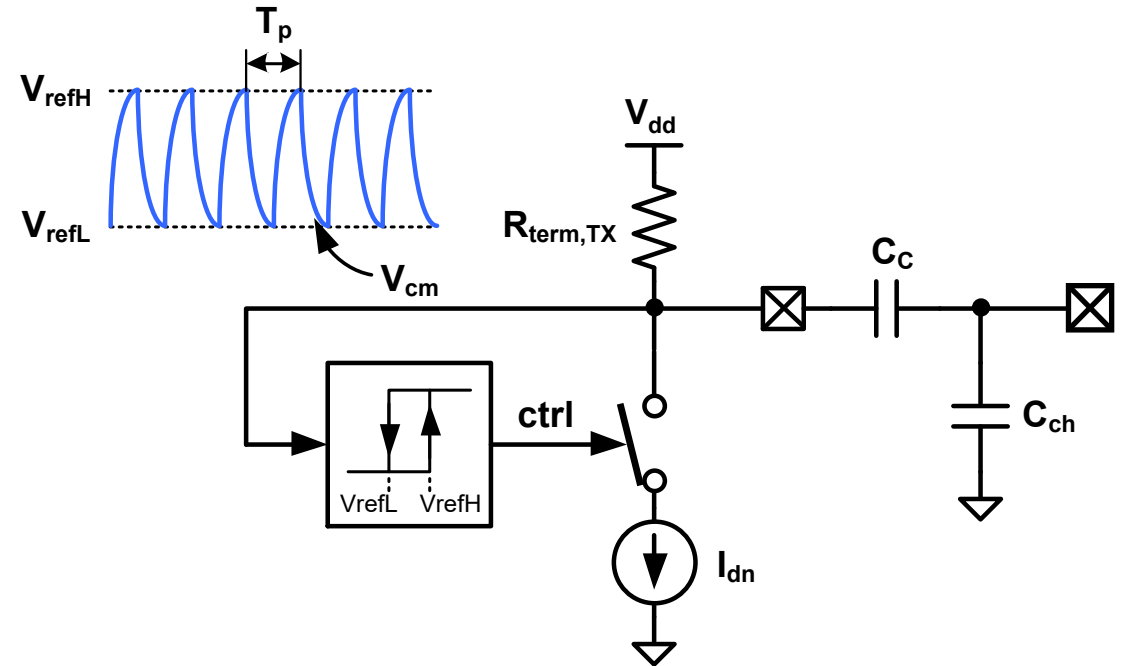
# RX Detection Circuit Example: Idea


- Transforms the transmitter into a relaxation oscillator and measures its oscillation period
  - With the TX pull-down current ( $I_{dn}$ ) off, the TX common-mode output ( $V_{cm}$ ) rises toward the supply voltage  $V_{dd}$
  - When  $V_{cm}$  reaches  $V_{ref,H}$ ,  $I_{dn}$  is switched on and  $V_{cm}$  starts falling
  - When  $V_{cm}$  reaches  $V_{ref,L}$ ,  $I_{dn}$  is switched off and  $V_{cm}$  starts rising again



[2] C. Guo and F. Yang, "Method and Apparatus for Receiver Detection on a PCI-Express Bus", US Patent US7222290B2.

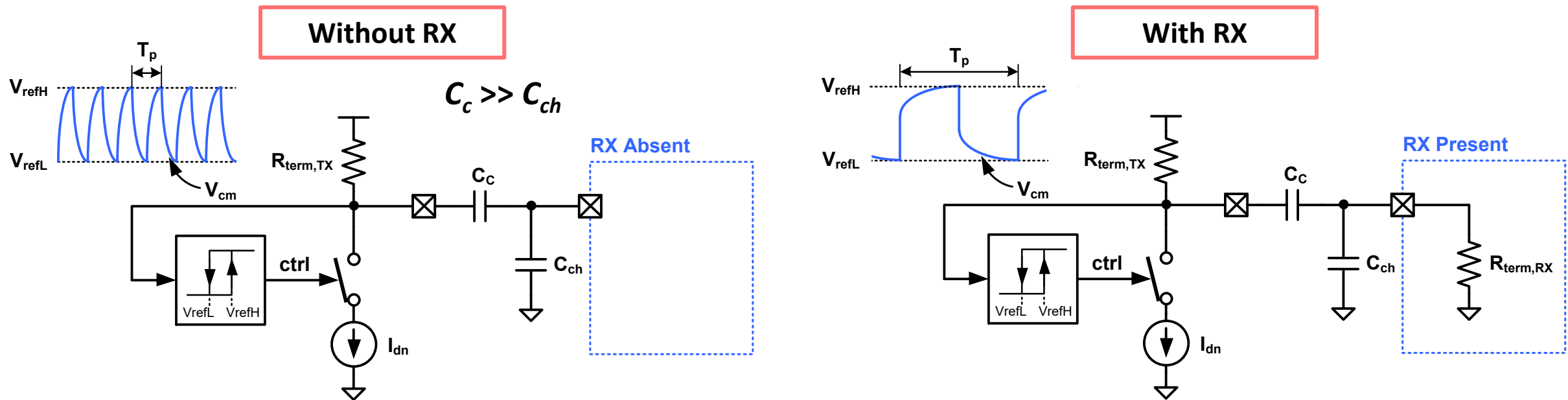
# RX Detection Circuit Operation

- The presence of RX can be detected based on the oscillation period
  - Without RX present:  $V_{cm}$  settles with  $\tau_{w/oRX} \approx R_{term,TX} \cdot C_{ch} \rightarrow$  **short periods**
  - With RX present:  $V_{cm}$  settles with  $\tau_{w/RX} \approx (R_{term,TX} + R_{term,RX}) \cdot C_c \rightarrow$  **long periods**


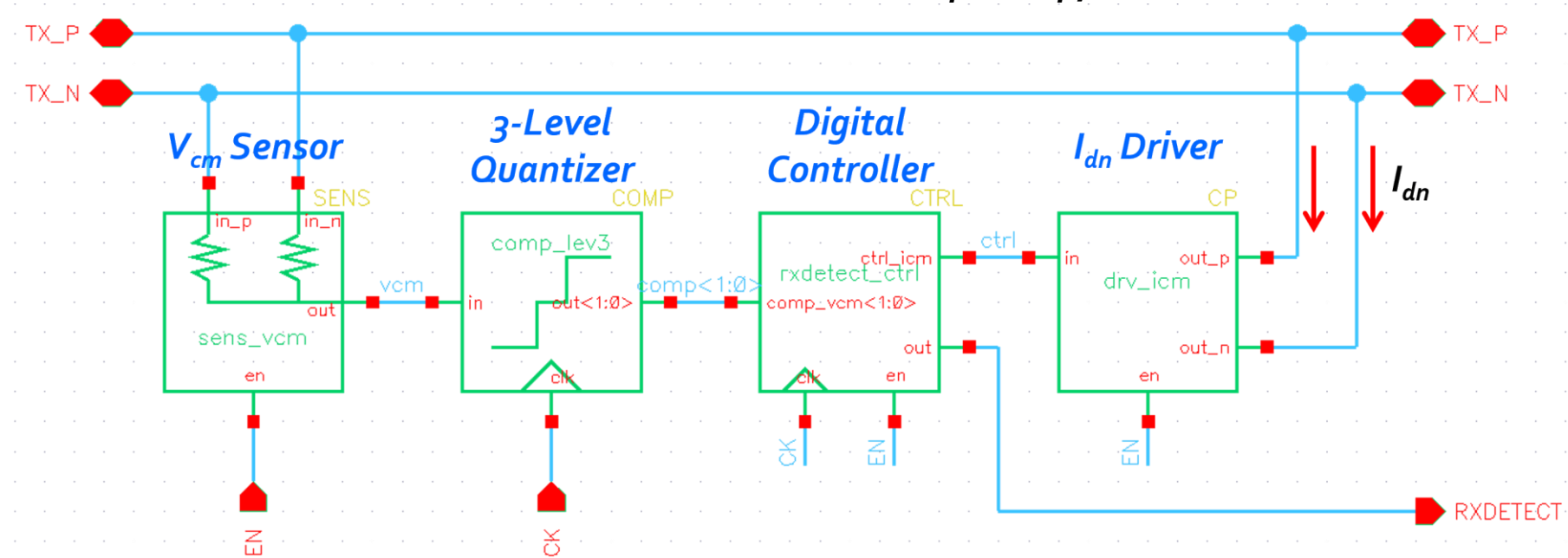
# RX Detection Circuit Implementation

- The RX detection circuit is a mixed-signal feedback loop with 4 components
  - A digital controller is inserted to measure the oscillation period in digital counts ( $N_p$ )
  - A receiver is considered to be present when  $N_p > N_{p,thres}$




# Design Margins of RX Detection Circuit

- The RX detection circuit must operate correctly for a range of condition parameter values:

$(C_{cl}, C_{ch}, R_{term,TX}, R_{term,RX})$

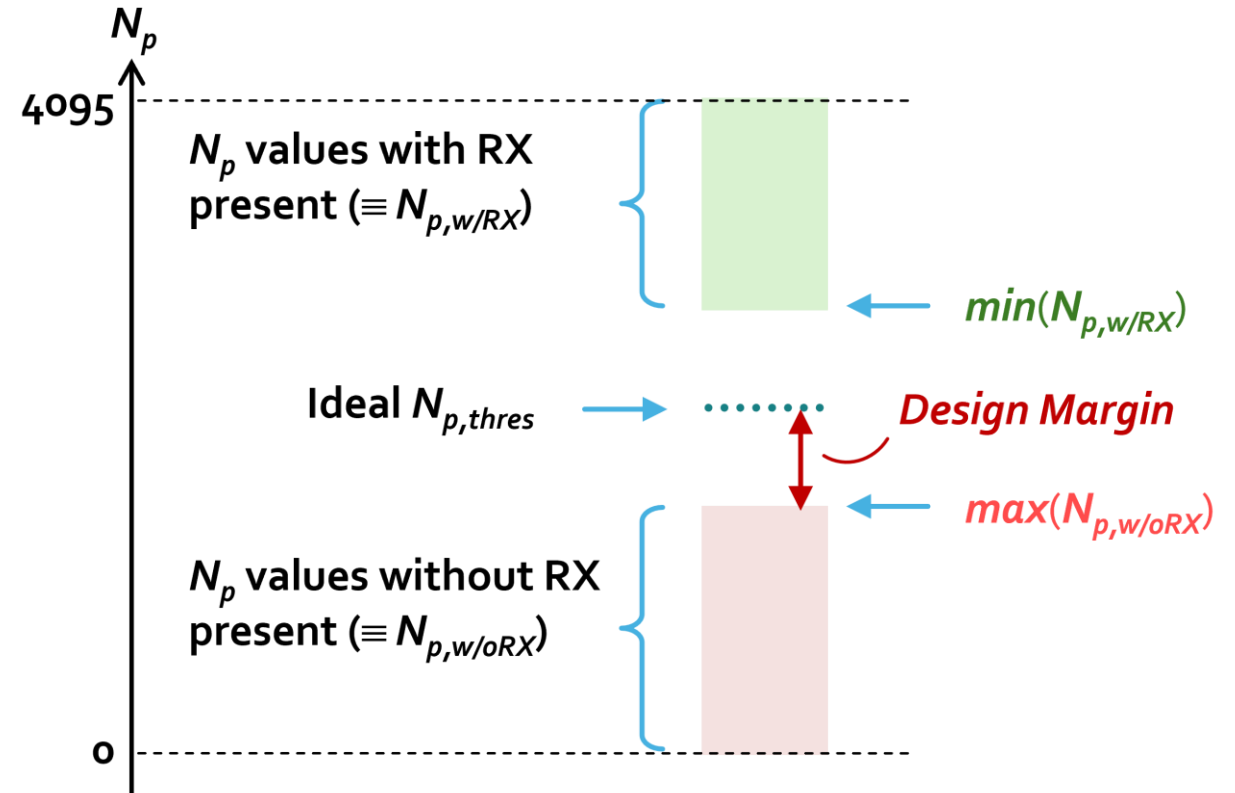- It implies that the oscillation period count ( $N_p$ ) will vary as well
- Minimum  $N_p$  with RX** must be sufficiently greater than **maximum  $N_p$  without RX**
- $\min(N_{p,w/RX}) > \max(N_{p,w/oRX})$





# Goal of This Work

- Build a UVM testbench that can characterize the design margin of a PCIe receiver detection circuit
  - What is the **min.  $N_p$  value with RX** across the range of condition parameters?
  - What is the **max.  $N_p$  value without RX** across the range of condition parameters?
- To achieve this, we need to:
  - Model the analog components of the PCIe transceiver in SystemVerilog; and
  - Find the min/max values of  $N_p$  by exploring a continuous-valued parameter space

# XMODEL Enables Analog in SystemVerilog/UVM


- *XMODEL* is a plug-in extension enabling ***fast and accurate analog/mixed-signal*** simulation in ***SystemVerilog***
  - ***Event-driven***: delivering 10~100x faster speed than Real-Number Model (RNM)
  - ***Analog***: supporting both functional and circuit-level models
  - ***SystemVerilog***: fully compliant with SystemVerilog-based flows (e.g. UVM)




 
# Event-Driven Simulation of Analog Circuits


- Using equation-based representation, *XMODEL* performs event-driven simulation of analog circuits in SystemVerilog



 
# Modeling Analog Circuits with *XMODEL* Primitives

- One can describe both signal-flow and conservative-system models of analog circuits by combining a rich set of *XMODEL* primitives

**Signal-flow Model**  
(Block-Level Model)



 
**Conservative-System Model**  
(Circuit-Level Model)




# Circuit-Level Modeling with *XMODEL*

- The circuit primitives of *XMODEL* allow one to model analog circuits by listing their elements directly in SystemVerilog
  - It's the most natural way to model nonlinear, switching, and loading effects


## Nonlinear Effects

 


## Switching Effects

 

## Loading Effects

 
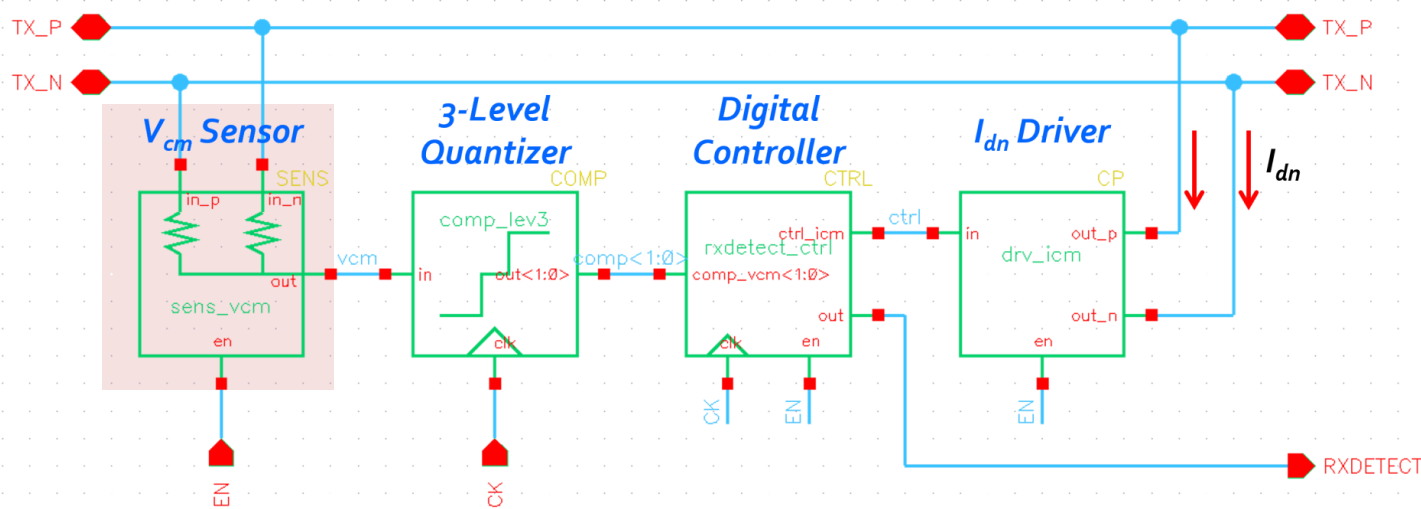
# RX Detection Circuit Model: $V_{cm}$ Sensor



## *sens\_vcm.sv*: TX common-mode sensor

```

module sens_vcm (
    output xreal out,
    input xreal in_p, in_n,
    input xbit en
);


xreal p0, n0;

switch    #(.R0(`INFINITY), .R1(10.0e3))
          SW1 (.pos(p0), .neg(out), .ctrl(en));
switch    #(.R0(`INFINITY), .R1(10.0e3))
          SW2 (.pos(n0), .neg(out), .ctrl(en));

endmodule // sens_vcm
  
```

- $V_{cm}$  **sensor** measures the common mode of the TX outputs with a pair of resistors when enabled
- Described using **switch** primitives
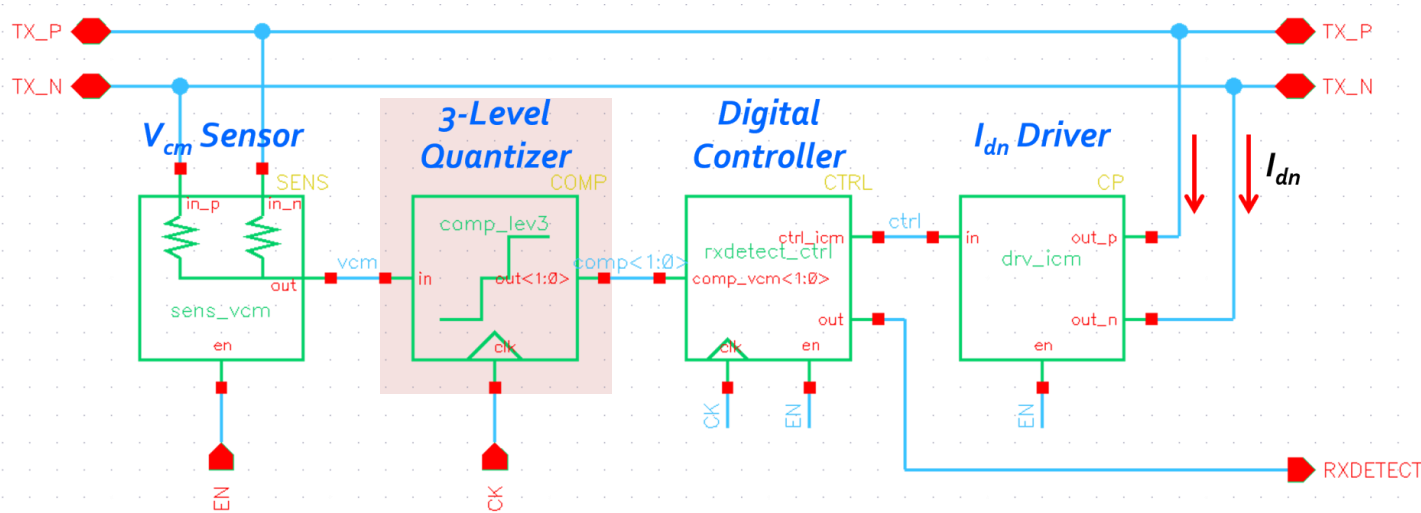
# RX Detection Circuit Model: 3-Level Quantizer



- **Three-level quantizer** digitizes  $V_{cm}$  into into a 2-bit code 00, 01, 11 by comparing it against  $V_{refL}$  and  $V_{refH}$
- Described using **compare** primitives

## *comp\_lev3.sv*: 3-level quantizer

```

module comp_lev3 #(
    parameter real VrefH = 1.75,
    parameter real VrefL = 1.35
) (
    output xbit [1:0] out,
    input xreal in,
    input xbit clk
);


    compare    #(.threshold(VrefL))
                COMP0 (.out(out[0]), .in(in),
                    .in_ref(`ground), .trig(clk));

    compare    #(.threshold(VrefH))
                COMP1 (.out(out[1]), .in(in),
                    .in_ref(`ground), .trig(clk));

endmodule    // comp_lev3

```
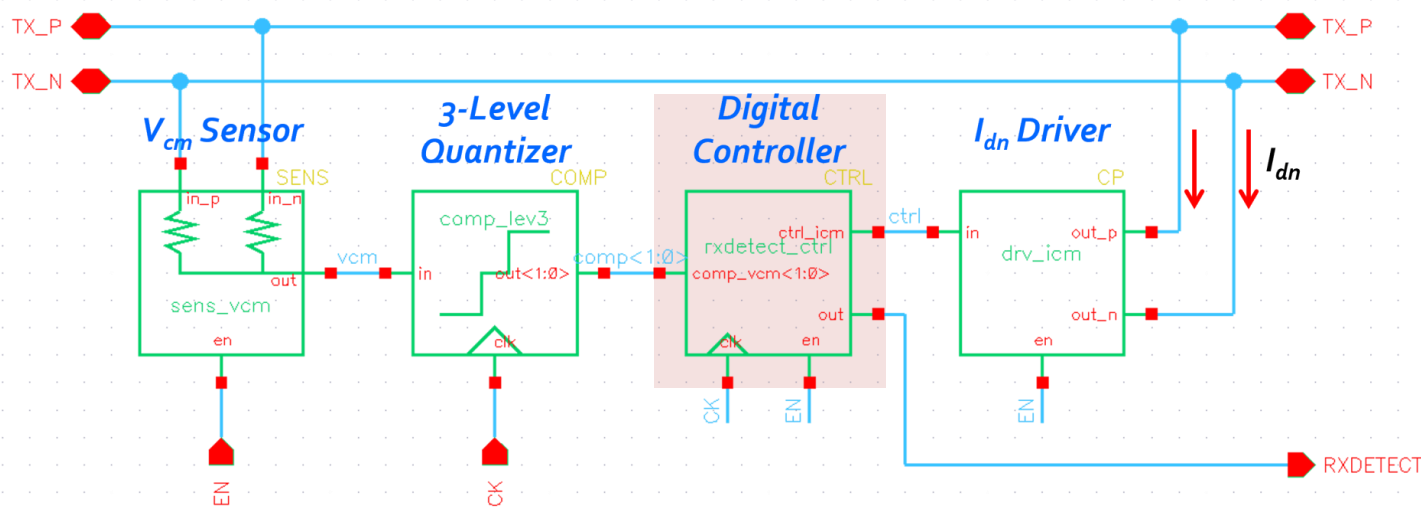
# RX Detection Circuit Model: Digital Controller



- **Digital controller** switches the TX currents ( $I_{dn}$ ) on or off based on the quantizer output and counts  $N_p$
- Described in pure Verilog

## *rxdetect\_ctrl.sv*: digital controller

```

module rxdetect_ctrl #(
    parameter int Np_thres = 1024
)()
    output reg ctrl_icm, out,
    input [1:0] comp_vcm,
    input clk, en
);


always @(posedge clk) begin
    if (!en) {ctrl_prev, ctrl_icm} <= 2'b00;
    else begin
        ctrl_prev <= ctrl_icm;
        if (comp_vcm == 2'b11) ctrl_icm <= 1;
        else if (comp_vcm == 2'b00) ctrl_icm <= 0;
    end
end

always @(posedge clk) begin
    if (!en) {Np_cnt, Tp_cnt, out} <= 16'b0;
    else if (!out) begin
        if (Np_cnt > 0) Tp_cnt <= (Tp_cnt < 12'bfff) ? Tp_cnt
        + 1 : 12'bfff;
        if (ctrl_prev && !ctrl_icm) begin
            if (Np_cnt < Np) Np_cnt <= Np_cnt + 1;
            else {Np_cnt, Tp_cnt, out} <= (Tp_cnt > Tp_thres)
            ? 16'b1 : 16'b0;
        end
    end
end
endmodule

```


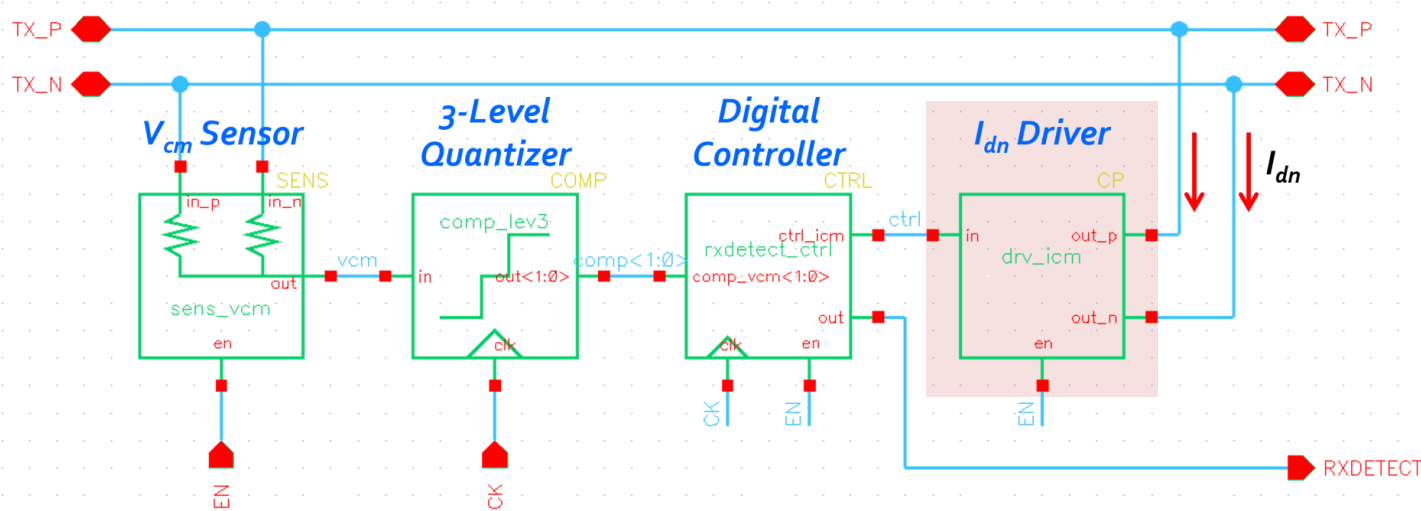
# RX Detection Circuit Model: TX Current Driver



- ***TX current driver*** pulls a common-mode current ( $I_{dn}$ ) from the TX outputs depending on the control input
- Described using ***transition*** & ***isource*** primitives

## *drv\_icm.sv*: TX current driver

```

module drv_icm #(
    parameter real Idn = 0.0125
) (
    output xreal out_p, out_n,
    input xbit in, en
);


xbit ctrl;

and_xbit    U0 (.out(ctrl), .in({in,en}));
transition  #(.value0(0.0), .value1(Idn))
            U1 (.out(i_dn), .in(ctrl));
isource     #(.mode("in"))
            IP (.pos(out_p), .neg(`ground), .in(i_dn));
isource     #(.mode("in"))
            IN (.pos(out_n), .neg(`ground), .in(i_dn));

endmodule // drv_icm
  
```
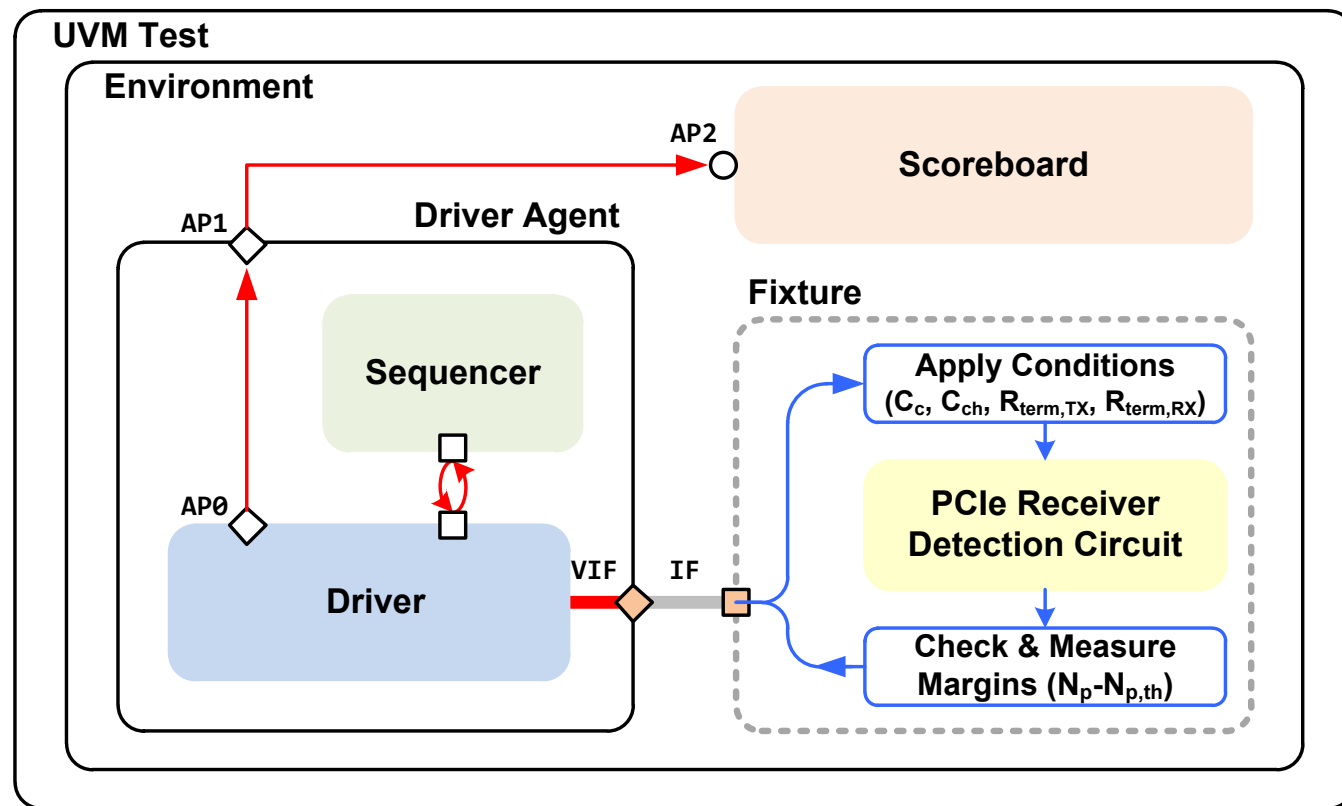
# UVM Testbench for Design Margin Exploration

- **Driver agent** searches for condition parameters that minimize or maximize  $N_p$
- **Fixture module** applies the condition parameters to the DUT and measures  $N_p$
- **Scoreboard** reports the min.  $N_p$  with the receiver present and max.  $N_p$  without



# Driver Agent

- Driver agent finds the optimal set of  $C_c$ ,  $C_{ch}$ ,  $R_{term,TX}$ ,  $R_{term,RX}$  that minimizes or maximizes  $N_p$ 
  - It uses reactive stimulus technique choosing the next parameter set using a Bayesian optimization
  - With these added DPI functions:
    - `BAYESOPT_initialize()`
    - `BAYESOPT_selectNext()`
    - `BAYESOPT_updateModel()`
    - `BAYESOPT_getOptimum()`

```
class SEQ_MARGIN extends uvm_sequence #(PACKET);
  `uvm_object_utils(SEQ_MARGIN)
  ...
  task body();
    PKT = PACKET::type_id::create("PKT");
    opt_data = BAYESOPT_initialize(4, lower_bounds, upper_bounds);

    // with receiver present
    PKT.RX_present = 1;
    for (int i=0; i<=num_iter; i++) begin:LOOP1
      if (i < num_iter) BAYESOPT_selectNext(opt_data, var_value);
      else BAYESOPT_getOptimum(opt_data, var_value);
      PKT.Cc = var_value[0];
      PKT.Cch = var_value[1];
      PKT.Rterm_tx = var_value[2];
      PKT.Rterm_rx = var_value[3];

      start_item(PKT);
      finish_item(PKT);
      get_response(RSP);

      // find minimum Np when receiver is present
      BAYESOPT_updateModel(opt_data, var_value, RSP.Np);
    end: LOOP1

    // with receiver absent
    ...
  endtask: body
endclass: SEQ_MARGIN
```

# Fixture Module

- Fixture module uses a handshaking protocol to enable multiple  $N_p$  trials within one simulation run
  - It waits for the driver agent to assert **START**;
  - Retrieves a new set of  $C_{ci}$ ,  $C_{ch}$ ,  $R_{term,TX}$ ,  $R_{term,RX}$  values and a flag to connect RX;
  - Enables the RX detection circuit and waits for its response; and
  - Sends the  $N_p$  value back to the driver agent and assert **DONE**

```

module FIXTURE (IF_t IF);
// interface handshaking
always begin: LOOP
    @(posedge IF.START);
    IF.DONE = 0;
    RX_present = IF.RX_present;
    Cc = IF.Cc;
    Cch = IF.Cch;
    Rterm_tx = IF.Rterm_tx;
    Rterm_rx = IF.Rterm_rx;

    EN = 0;
    #(t_init);
    EN = 1;
    fork
        @(posedge RXDET.CTRL.DONE);
        #(t_meas);
    join_any
    disable fork;

    IF.Np = (RXDET.CTRL.DONE) ? RXDET.CTRL.Np_val : -1;
    IF.DONE = 1;
end: LOOP

```

## Fixture Module (2)

- Testbench configurations include:
  - RX detection circuit (DUT)
  - TX driver with AC-coupled channel
  - RX front-end with ideal switches controlling its presence
  - Clock and supply sources
- Using *cap\_sw* & *res\_sw* primitives to change  $C_{cl}$ ,  $C_{ch}$ ,  $R_{term,TX}$ ,  $R_{term,RX}$  as signals (i.e., not parameters) during simulation

```
// DUT model for the PCIe receiver detection circuit
rxdetect    #(.VrefH(VrefH), .VrefL(VrefL), .Np_thres(1024))
             RXDET (.CK(CK), .TX_P(TX_P), .TX_N(TX_N),
                  .EN(EN), .RXDETECT(RXDETECT));

// transmitter and AC-coupled channels
tx_pcie     TX (.out_p(TX_P), .out_n(TX_N), .vdd(VDD),
               .Rterm(Rterm_tx), .Cp(Cp_tx));
channel     CHN_P (.port_1(CH_P), .port_2(RX_P), .Cch(Cch));
channel     CHN_N (.port_1(CH_N), .port_2(RX_N), .Cch(Cch));
cap_sw      CP (.pos(TX_P), .neg(CH_P), .C(Cc));
cap_sw      CN (.pos(TX_N), .neg(CH_N), .C(Cc));

// add receiver depending on RX_present
bit_to_xbit RX_CONN (.in(RX_present), .out(RX_EN));
switch      SW0 (.pos(RX_P), .neg(RX_P0), .ctrl(RX_EN));
switch      SW1 (.pos(RX_N), .neg(RX_N0), .ctrl(RX_EN));
rx_pcie     RX (.in_p(RX_P0), .in_n(RX_N0),
               .Rterm(Rterm_rx), .Cp(Cp_rx));


// sources feeding clock and supply voltage
clk_gen     #(.freq(f_clk)) XP0 (.out(CK0));
xbit_to_bit CK_CONN (.in(CK0), .out(CK));
dc_gen      #(.value(vdd_val)) XP1 (.out(VDD));
```

endmodule
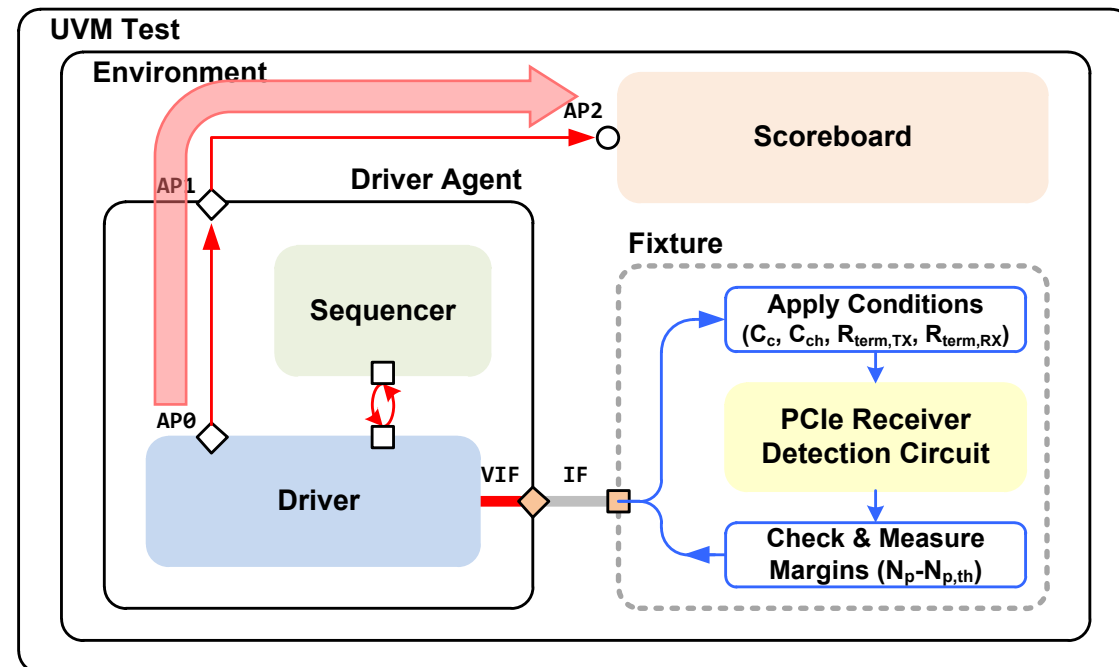
# Scoreboard Component

- It listens to all the  $N_p$  results broadcast by the driver agent and keeps track of  $\min(N_{p,w/RX})$  &  $\max(N_{p,w/oRX})$
- And reports these values when the simulation is finished

-----  
 Min  $N_p$  with RX present = 2507  
 Max  $N_p$  with RX absent = 223  
 -----





# Experimental Results: Measuring $N_p$

- Collecting  $\min(N_{p,w/RX})$  &  $\max(N_{p,w/oRX})$  for various  $V_{refH}$  &  $V_{refL}$  values
- Each simulation takes about 90 seconds to complete 400 iterations

$V_{refL} \backslash V_{refH}$	1.700	1.725	1.750	1.775
1.400	(15, 151)	(29, 175)	(55, 203)	(1187, 255)
1.375	(15, 167)	(36, 183)	(663, 215)	(3791, 259)
1.350	(27, 179)	(499, 199)	<b>(2507, 223)</b>	(4095, 271)
1.325	(355, 207)	(1959, 223)	(3851, 247)	(4095, 283)
1.300	No Oscillations	No Oscillations	No Oscillations	No Oscillations

# Experimental Results: Design Margins

- Design margin is calculated as  $(\min(N_{p,w/RX}) - \max(N_{p,w/oRX})) / 2$
- Design margin is highly sensitive to the variations in  $V_{refH}$  and  $V_{refL}$

$V_{refL} \backslash V_{refH}$	1.700	1.725	1.750	1.775
1.400	-68	-73	-74	466
1.375	-76	-73	224	1766
1.350	-76	125	<b>1142</b>	1912
1.325	64	868	1802	1906
1.300	-	-	-	-

# Summary

- A UVM testbench for characterizing the design margins of an analog/mixed-signal circuit is presented
- The testbench finds the worst-case deviation of the circuit's response across a continuous-valued parameter space by:
  - Using *XMODEL* primitives to model the analog components of a PCIe receiver detection circuit at the device level; and
  - Combining a reactive stimulus technique with a Bayesian optimization algorithm to efficiently and adaptively explore the parameter space
- This work paves the way for adaptive, coverage-driven AMS verification